
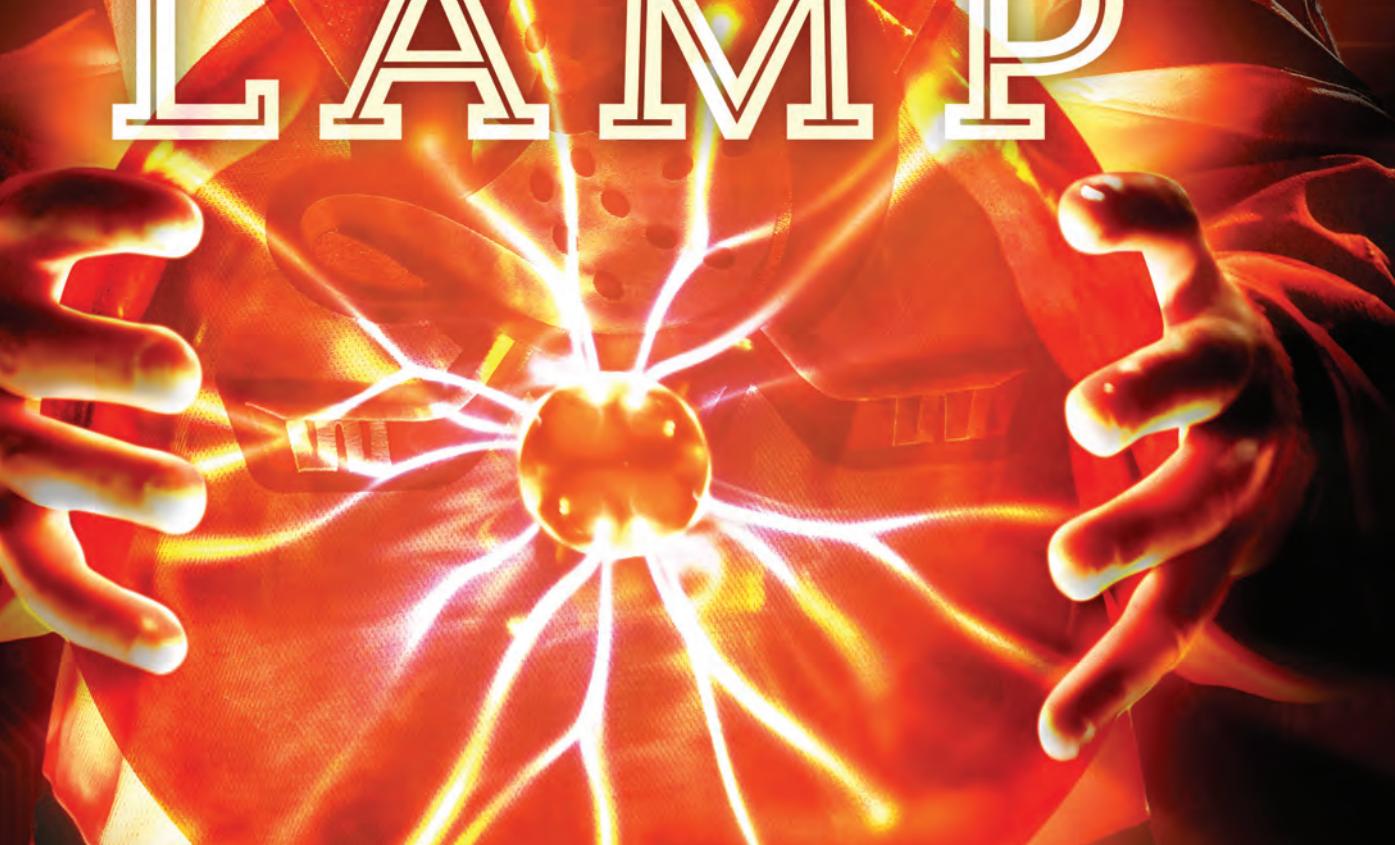


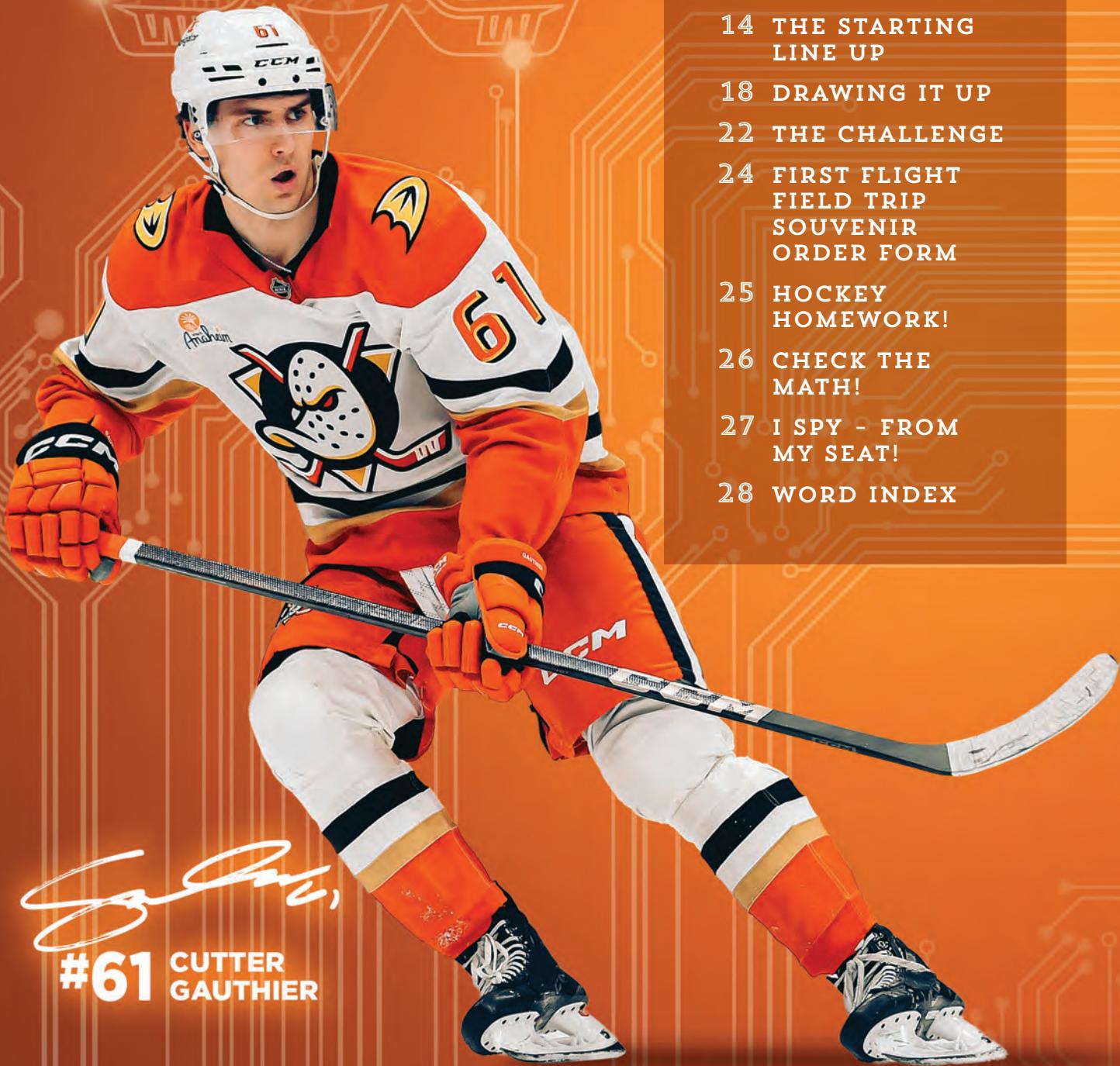

# LIGHT THE LAMP

visit  
Anaheim





## TABLE OF CONTENTS

- 2 LIGHT THE LAMP
- 3 THINK LIKE AN ENGINEER
- 4 IT'S ELECTRIC
- 9 THE ELECTRIC PLAYGROUND
- 14 THE STARTING LINE UP
- 18 DRAWING IT UP
- 22 THE CHALLENGE
- 24 FIRST FLIGHT  
FIELD TRIP  
SOUVENIR  
ORDER FORM
- 25 HOCKEY  
HOMEWORK!
- 26 CHECK THE  
MATH!
- 27 I SPY - FROM  
MY SEAT!
- 28 WORD INDEX



# LIGHT THE LAMP


There's nothing more exciting than a goal scored by the home team. When the Ducks score you better be ready for something special to happen at Honda Center. A horn fills the arena with sound, a goal song blasts from speakers throughout the building, and intense red light flashes behind the goal. This electrifying event is known to Ducks players and fans as "Lighting the Lamp". While the puck entering the net sets off this chain of events, it's electricity, shooting through a vast series of circuits, that makes it all happen.

You probably already know this but, electricity makes a lot of the things we do each day possible. It powers the lights in our homes and the mobile devices we use to play the newest games or to say "Hey!" to a friend. Electricity can be found almost everywhere and Honda Center is no exception. We want you know how it works and to do so, you'll go on a journey to light your lamp. The information in this workbook will teach you to think like an electrical engineer. By the end of this book you'll design and build a circuit that powers a light and sets off sound just like an Anaheim Ducks goal.

It will take your best effort and some perseverance to work through this book, not to mention teamwork. But, once you do, you'll be ready to take on the challenges that await you during the First Flight Field Trip. When it comes to hockey, the best goals take teamwork, hard work, creativity, and skill.

***Do you have what it takes  
to "Light the Lamp"?  
We know you do!  
Let's get started!***


Dedicated to J.H.<sup>2</sup>

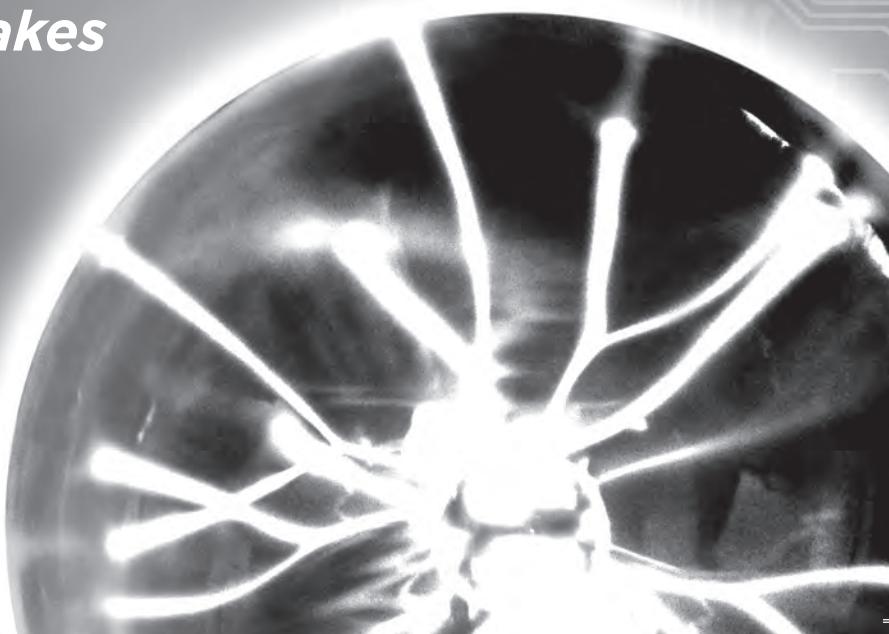
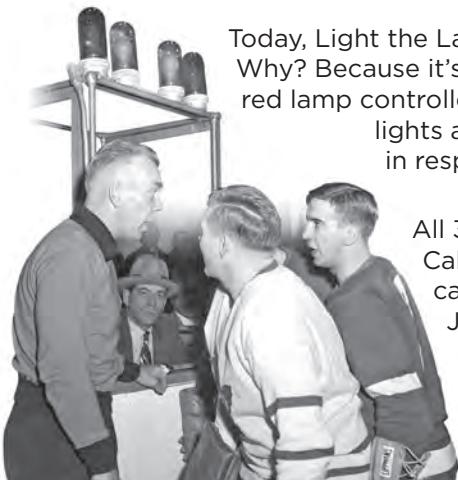
# LIGHT THE LAMP

The term Light the Lamp has been used in hockey ever since the early days of the game. When it became a spectator sport back in the early 1900's, Light the Lamp had a very different meaning because electricity wasn't available everywhere as it is now. NHL arenas didn't have access to lasers or smoke machines, nor did they have fog horns or goal songs blasting through the speakers. What they did have was a lamp installed behind the goaltender. This light was controlled by a goal judge who would turn it on only after the puck had gone past the goaltender, crossed the goal line, and entered the goal. A flashing red light would indicate to everyone in the arena that a goal had been scored!

Today, Light the Lamp is the event that fans look forward to when they attend a hockey game. Why? Because it's a celebration for a home team goal! At the heart of this celebration is still a red lamp controlled by a goal judge. But now, there's a whole lot more! A multitude of flashing lights and sounds are also used to give fans more reasons to scream, shout, and sing in response to their team's accomplishment on the ice.



All 32 teams across the league Light the Lamp in their own creative ways. The Calgary Flames fill the arena with red lights. The Columbus Blue Jackets shoot cannons. And, the Edmonton Oilers blow fire out of an oil rig up in the rafters. Just about every fog horn, every goal song, and every red lamp is unique. When the Anaheim Ducks score a goal, a loud siren, fog horn, and laser light show fill Honda Center. If you're a Ducks fan, this is the best thing in hockey!

Hockey often uses technology to improve the game for its fans. From hockey sticks to the ways people can interact with players using social media, lighting the lamp is no different. So, what will Light the Lamp look like in the future? The possibilities are limitless! Regardless, every light and every sound will still be powered by electricity and connected by circuits. It's time to learn about these things because **you are the engineer** we need to improve this important aspect of the game. How will you use your creativity to Light the Lamp?

**THIS IS YOUR INVITATION TO INNOVATE!**




**LAMP HISTORY**

# THINK LIKE AN ENGINEER



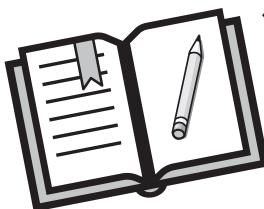**Helmets are essential for the game of hockey. In order to think like an engineer you'll also need some equipment.**



## JOURNAL

Engineers use journals or notebooks to record their ideas, collected data and calculations to read them again later. Each time you see this icon, write down some notes or any observations about electricity in your journal. If you like to draw, sketching plans and diagrams is encouraged.

## PENCIL & ERASER

Engineers and scientists like to take notes that are very neat. That's why they use pencils and erasers for the best results. It's important to keep your ideas or notes, no matter how wild and crazy they are. Erase mistakes, not ideas!

**DON'T HAVE A JOURNAL?**  
*Scan the QR CODE for First Flight Resources to learn how to make one.*



**JOURNAL**

## AVENGER OR ENGINEER?

The heroes and villains from the movies that take place in a galaxy far, far, away seem to use electricity with such ease. They're able to stop lightning bolts out of midair or even shoot them out of their fingertips. Although this is make believe, there are in fact, real people who have the special ability to do amazing things with electricity. Who are they? They're electrical engineers! These men and women are behind countless everyday products and are able to make our lives better by harnessing the power of electricity. They can control it to turn motors, send digital messages through the air, and do thousands of other cool things. Most of all, we're fortunate that these engineers use their "powers" to turn on millions of light bulbs, keeping us out of the dark... side.



There are many types of electrical engineers, each specializing in using electricity for good. Match the objects in the box to the engineer who most likely built it. Use a dictionary or books on this topic to help you complete this activity! Then, in a journal, write down the type of electrical engineer that interests you the most.




**Computer Engineer**



**Power Engineer**



**Microelectronics Engineer**

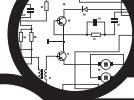


**Circuits Engineer**



**Telecommunications Engineer**



**Information Technology Engineer**

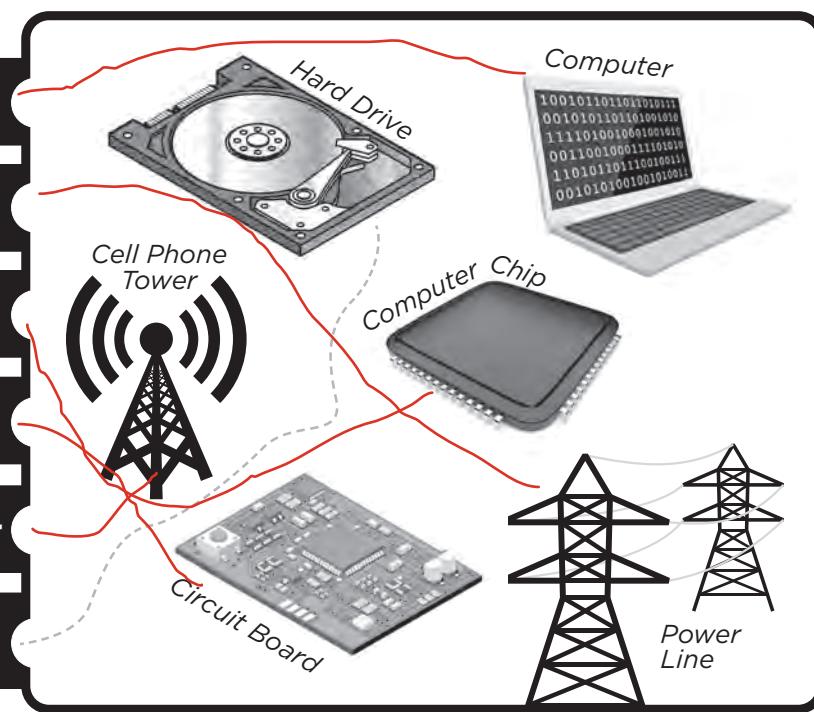



# IT'S ELECTRIC


## ! READ THIS FIRST!

All the experiments in this workbook use safe, low-voltage batteries and should be done with adult supervision. **PLEASE DO NOT** use electricity from a wall outlet for any of these activities. This type of electricity is high voltage that could cause serious injury. Let's respect electricity so that we can have a fun and safe time Lighting the Lamp!

The atmosphere at a Ducks game is electric—just like electricity itself! This powerful energy keeps our homes cozy, our gadgets running, and our world bright. Imagine life without lights, cars, or computers—no thanks! Thanks to electrical engineers, we have electricity everywhere we go, from home and school to the Honda Center.
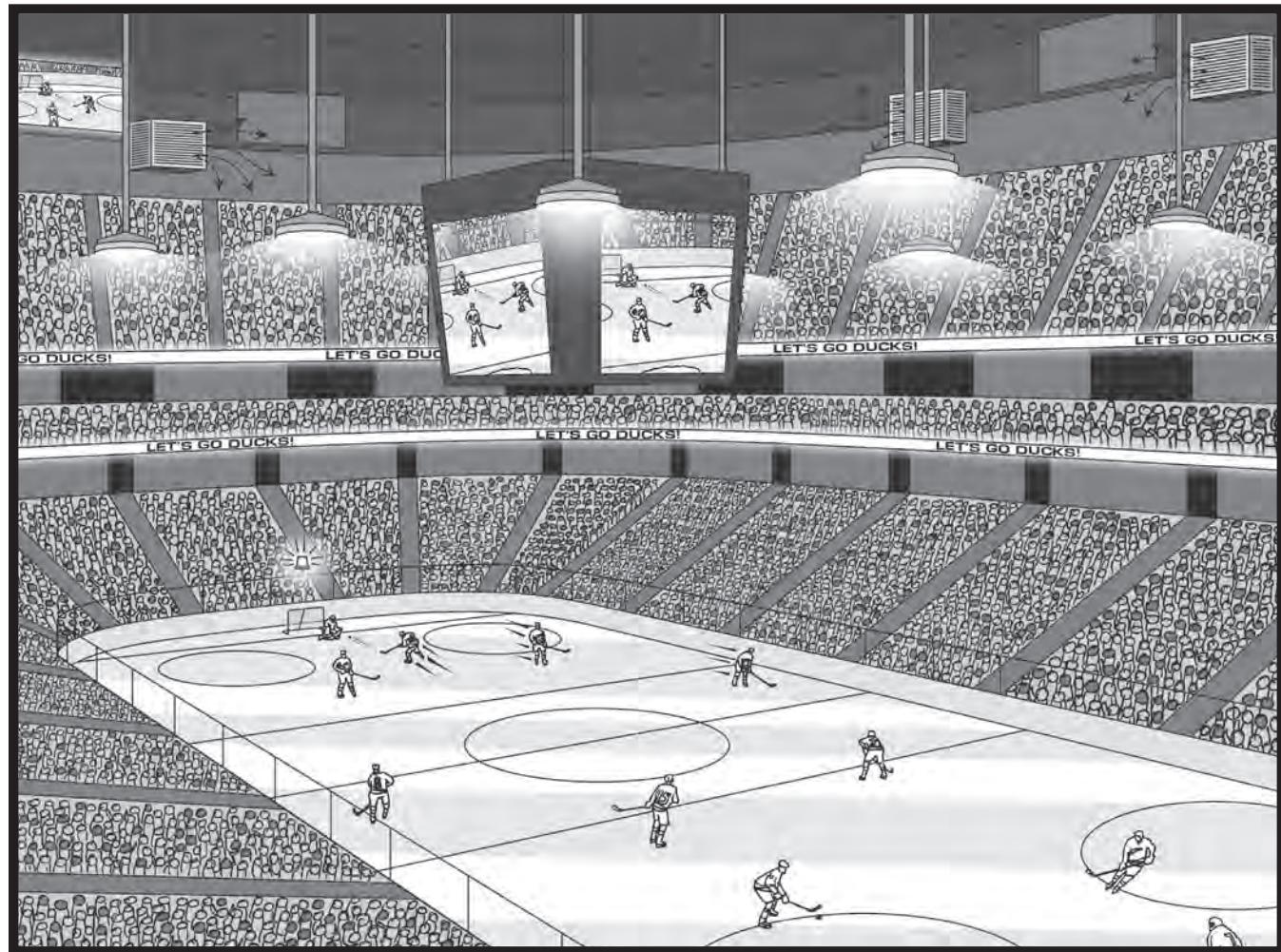
## COACHES CHALLENGE

Take a look at Honda Center and circle as many things in the picture that use electricity. In your journal, write down how you think electricity makes these things work at this hockey game.



# IT'S ELECTRIC




We don't usually think much about electricity except when we plug things into an outlet. But where does it really come from? Some electricity comes from power plants that use water, coal, or sunlight. But electricity has actually always been part of nature.

Have you ever seen lightning in a storm? That's electricity! Electric eels can also make electricity to shock other animals. Even inside your own body, electricity is at work. It helps your brain and nerves send messages. When you stub your toe, electricity carries the "ouch" signal to your brain so you can feel it.

Scientists only learned how electricity works a little over 100 years ago. They discovered it comes from atoms. Atoms are the tiny building blocks of everything around us. You can't see them with your eyes, but special tools show they're made of even smaller parts called protons, neutrons, and electrons. This tiny team of particles works together to make electricity possible—and that's how we use it every day!

It was just a little over 100 years ago that scientists figured out the nature of electricity. Most importantly, they learned how to control it. These really smart people found that the **atom** was behind this magic. Atoms are everywhere and in everything. They are the small building blocks of life that are too small to see with your eyes. With special equipment, you'll find that they're made of even tinier things called **protons, electrons, and neutrons**. These **teams of particles** have many different properties and their special relationship with each other is what we use to make electricity work for us!

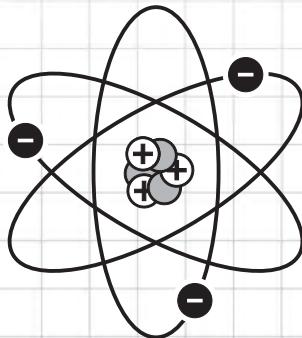

**Protons and electrons each carry their own type of electrical energy. This is called charge.**



Protons have a positive (+) charge



Electrons have a negative (-) charge




Neutrons do not have a charge

**Particles have a unique relationship with each other. There is an invisible (electric) field that wants to keep them together or apart!**

Opposite charges are attracted to each other. This is where the phrase "opposites attract" comes from!



Like charges repel

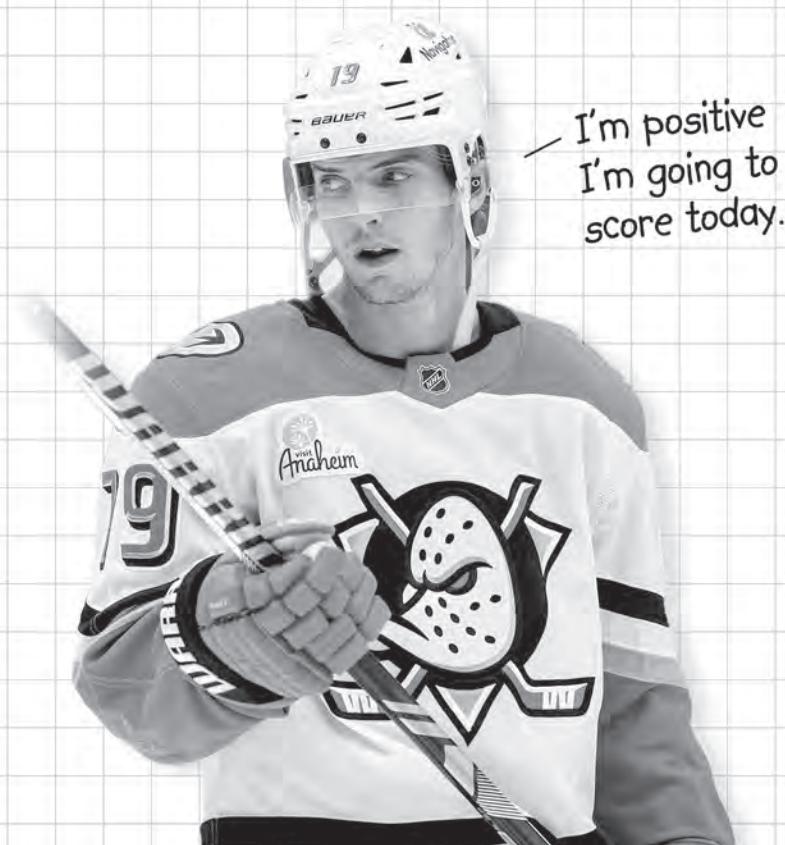



# IT'S ELECTRIC

## SPECIAL TEAMS


Everything around us is made of atoms—so tiny you can't see them, even with your eyes wide open! Atoms have smaller parts inside them called protons (with a + charge) and electrons (with a - charge).

- When an atom has the same number of protons and electrons, it is neutral (no charge).
- When an atom has more electrons, it is **negatively charged**.
- When an atom has more protons, it is **positively charged**.

Think of it like a hockey game: when both teams have the same number of players, it's fair. But when one side has more, the game changes!




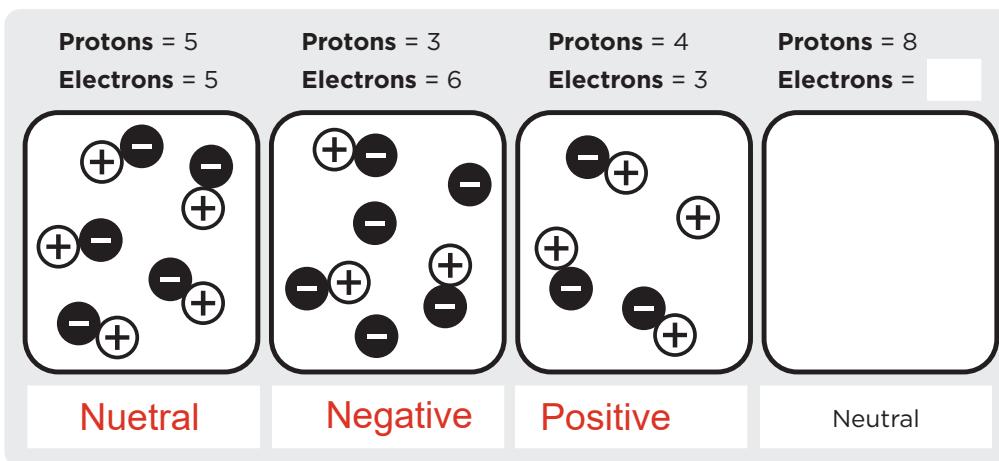Take a look at the pictures to the right and label each cell positively charged, negatively charged, or neutral. Then, draw your own picture using the information that's given to you.



In an NHL game, only 5 skaters and 1 goalie from each team are allowed on the ice at the same time. When both teams have the same number of players, that's called **even strength**.

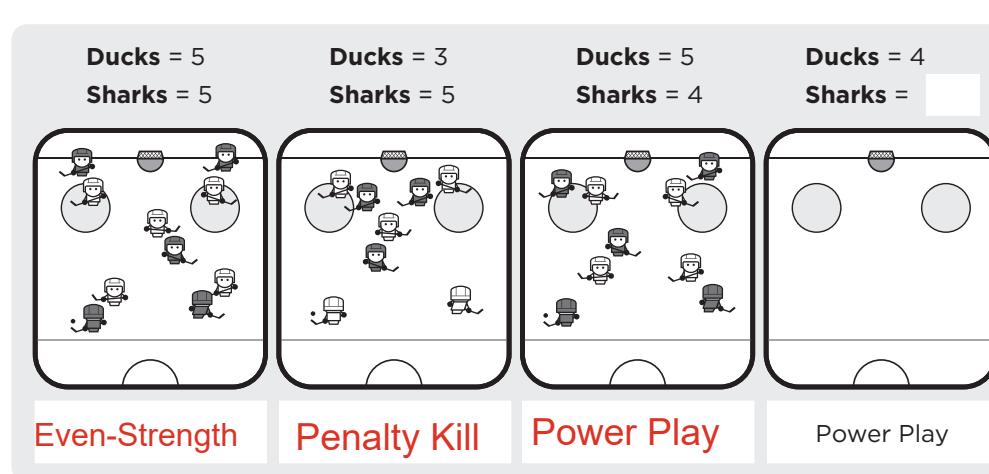But when a player breaks a rule, they sit in the penalty box. This leaves one team with more players on the ice. That's called a **power play** for the team with more players, and a **penalty kill** for the team with fewer players.



= Ducks (Home Team)



= Sharks (Away Team)



## COACHES CHALLENGE

Take a look at the pictures to the left and write down whether the home team Ducks are on the power play, penalty kill, or even strength. Then, draw your own picture using the information that's given to you.

POWER  
PLAY



# IT'S ELECTRIC



In hockey, moving the puck using the skill of passing often leads to speedy rushes up the ice or incredible goals. This is the thing that Anaheim Ducks fans love to see. It's no different with electricity. Amazing things happen when electrons move. When they do, it generates two types of electricity - **static electricity** and **current electricity**.

## STATIC ELECTRICITY

**Static electricity** is a build-up of electrons on the surface of an object. Although this happens all around us, we don't realize it exists until we touch something made of metal. The shock you feel, hear, or even see is the result of static electricity on your body. So how does this happen? The best way to explain this is through our most common run-in with static electricity.

### A Static Electricity By Adhesion


Electrons move by sticking onto another object. When two neutral objects are rubbed together, electrons can break free from one object and adhere, or stick, to the other.

### B Static Electricity by Conduction

Electrons move through touching. The electrons from a negatively charged object will disperse all over a neutral object when they touch.
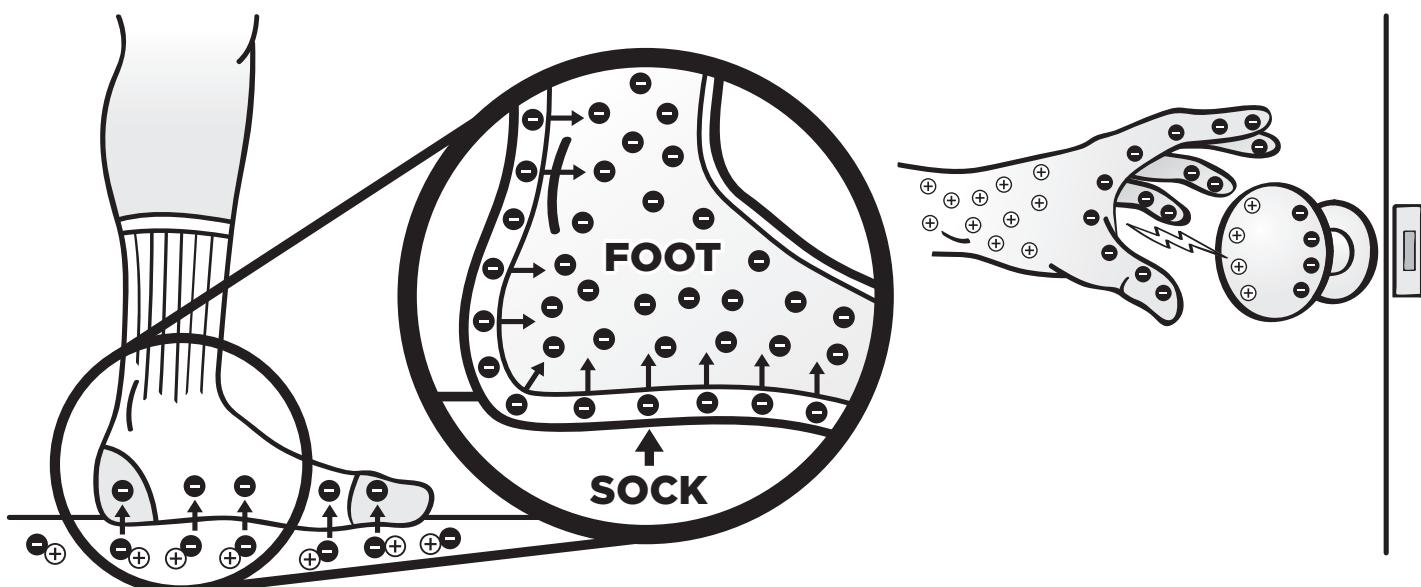
### C Static Electricity by Induction

Induction is the movement of electrons by the repelling and attracting nature of atomic particles.



When you walk on carpet, electrons jump from the carpet to your sock, giving you a charged-up sock!

When your sock touches your skin, electrons move onto you, making your body charged all the way to your fingertips!

When your hand gets close to a metal doorknob, the electrons on your skin are pushed toward it. That's why you feel a little shock—the electrons are jumping to join the protons in the doorknob!



What other places have you observed static electricity in your classroom or school?



# IT'S ELECTRIC






Complete the “hair raising” activities below to see, feel, and hear static electricity at work.

**Step 1: Gather** Materials

- Blown up balloon
- Bed head

**Step 2:** Try the activities found in pictures **A**, **B**, and **C**. Start with **A**. Then, for **B** and **C**, you'll need to charge up the balloon first before doing these activities.

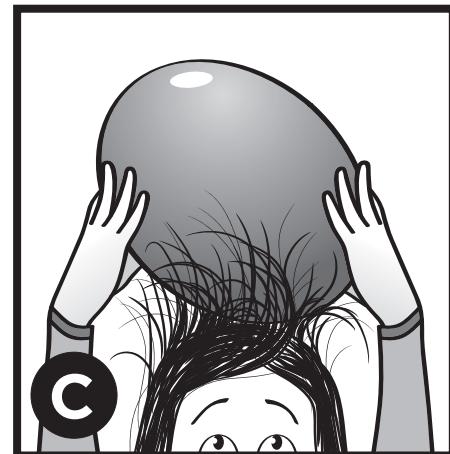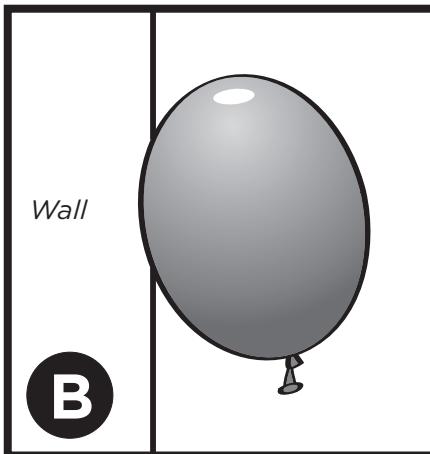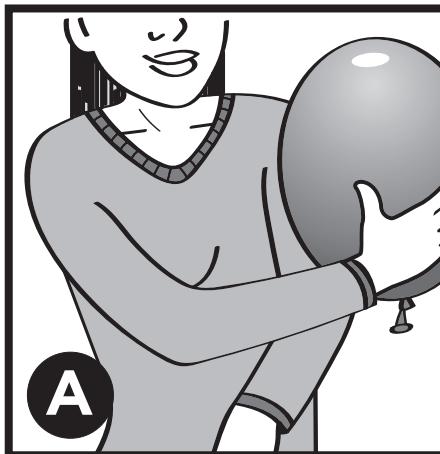**Step 3:** Write your observations for each activity in the space provided or in your journal. How did you experience static electricity and where did you see static electricity by adhesion, conduction, and induction?




There will be varied representations of static electricity in each frame  
Adhesion/Conduction      Adhesion/Induction      Adhesion/Induction
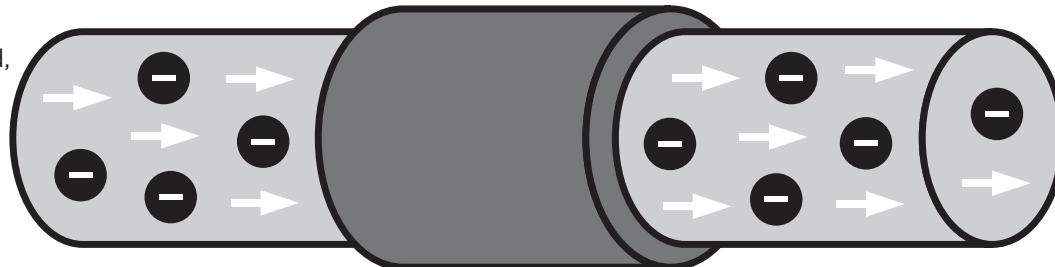
## CURRENT ELECTRICITY

Static electricity goes away, or discharges, very quickly. While it can provide a large amount of electricity, we need something else that can power the lights and our devices for long periods of time. **Current electricity** is the answer! Current electricity is what you get when there's a continuous, or non-stop, flow of electrons through an object. Thanks to electrical engineers, we can create this flow of electrons using generators that push them safely to people's homes near and far. The best thing about current electricity is that we can control it using a circuit, the electric playground for electrons!

The rate, or speed, of electron flow is measured in **amperes (A)**.




# THE ELECTRIC PLAYGROUND


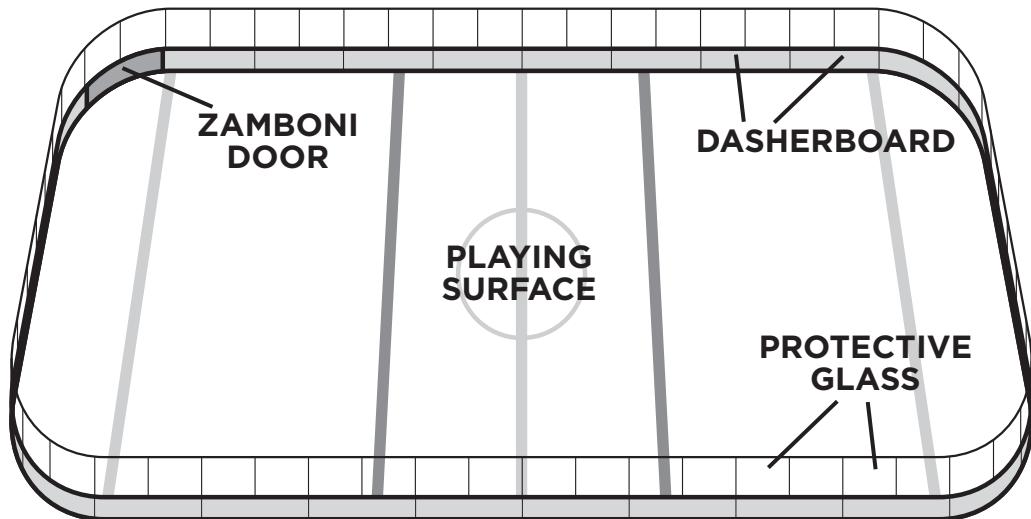
## THE ICE RINK

No other sport in the world has anything like the hockey rink. That's because no sport uses an object as dynamic as a hockey puck. From its shape to the materials it's made of, everything about the **ice rink** was made for hockey. It keeps the spectators safe, allows for physical play, and most of all, it's the place where the puck can move at a fast and exciting pace. **Let's learn about the things that make up this frozen playground.**



### DASHERBOARD

A series of about 70 rink segments called **dasherboards** are connected side-by-side in the shape of a hockey rink. Each one is 96 inches long and 40 inches tall.

### PLAYING SURFACE

This is the one-inch thick ice sheet that makes up the foundation of the ice rink. The parallel lines that run across the width of an ice rink divides it into three zones - offensive, defensive, and neutral.

### PROTECTIVE GLASS

A piece of half-inch thick acrylic glass sits on top of each dasherboard. They keep the puck in play and protect the fans from most slap shots and high speed collisions.

### MATERIAL

Dasherboards are made of a durable but elastic material that helps the puck keep its speed each time it bounces off of the rink walls.

### ZAMBONI DOOR



This segment can be opened or closed. When the **door is open**, the large gap it creates allows the Zamboni ice resurfacing machine to enter the rink. The game can only resume when the **door is closed**. This completes the rink's shape again.
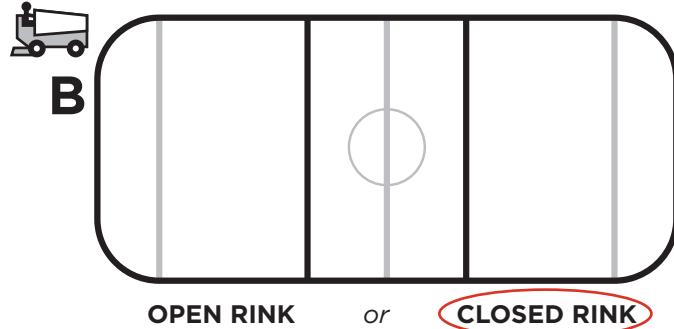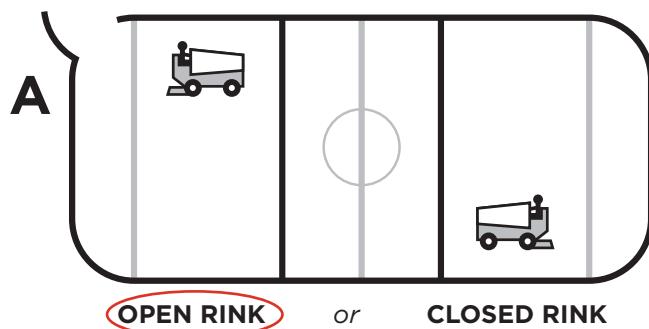
### SHAPE

The ice rink is formed in a complete loop and without any gaps. Its shape keeps the puck and players safely inside the rink.



Identify the two types of ice rinks when the Zamboni door is at positions **A** and **B**. Circle the correct answers below.





# THE ELECTRIC PLAYGROUND


The electron is an atom's most dynamic particle because it loves to move! But, it's not until they all flow in one direction in a circuit does it become electricity we can use. From its shape to the materials it's made of, everything about a circuit is amazing. It gives electrons a path to follow and it connects components together so that we can do fun and exciting things with them.

Let's learn more about the things that make up this electric playground!
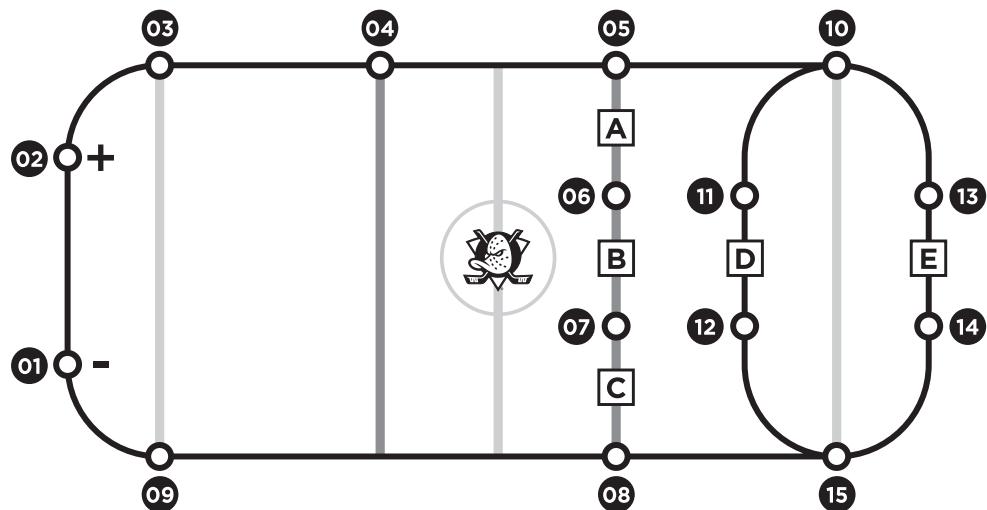
## THE CIRCUIT BOARD

Circuits can be found inside any item that requires electricity. They can be found in simple items like flashlights or very complex ones like computers. No matter what they look like, all circuits share the same basic rules. That includes the circuit that Lights the Lamp at Honda Center! The best way to learn about these rules is to start with a working circuit and then learn about the parts that form it. This type of backwards engineering has a name.

It's called **reverse engineering**. Let's engineer and reverse engineer your circuit!




### Step 1: Gather Your Materials

You'll need the following materials to engineer the Light the Lamp circuit. Before you get started, how do you think each item will be used?



Orange Wire \_\_\_\_\_

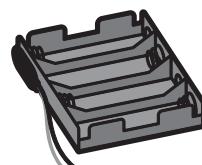


Battery Holder \_\_\_\_\_



9 Brass Fasteners \_\_\_\_\_




Red LED Bulb \_\_\_\_\_

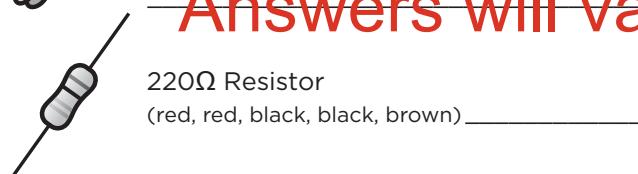


220 $\Omega$  Resistor  
(red, red, black, black, brown) \_\_\_\_\_



Scissors \_\_\_\_\_

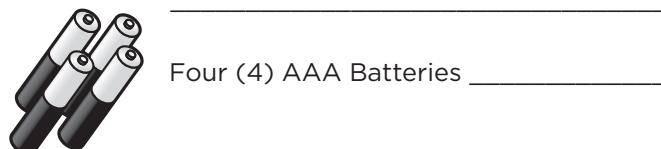

Four (4) AAA Batteries \_\_\_\_\_

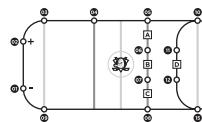

Light the Lamp  
Circuit Board \_\_\_\_\_

**Answers will vary**

# THE ELECTRIC PLAYGROUND




## Step 2: Attach Your Materials to the Circuit Board

Follow the instructions below to attach the battery, wire, resistor, and red LED using the terminals (or holes) numbered 01 to 09.

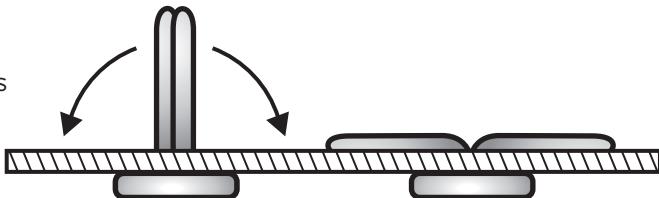
### A. Terminals @ 01, 02, 03, 04, 05, 06, 07, 08, and 09

- A terminal is the place where wires and components connect. Push a brass fastener through the holes numbered 01 to 09 and bend the tails on the other side of the circuit board to secure them tightly.



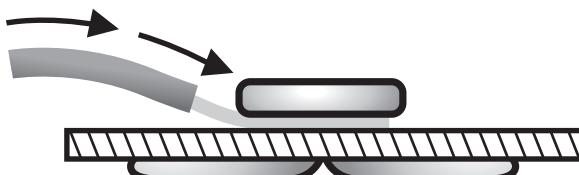
### B. Wires @ segments [02-03], [04 -05], [05-06], [07-08], [08-09], and [01-09]

- Measure the distance between the terminals and then add an inch to it before cutting each wire segment.
- Use scissors to remove the outer jacket from both ends of the wire. Read the box below to learn how to do this!
- Insert, or hook, each metal end of the wire under the heads of the brass fastener. Push it from underneath the board to make space for the wire.


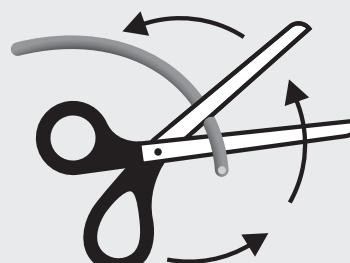
#### Stripping a Wire

There are fancy tools you can use to "strip" a wire but a pair of scissors will do the trick!



**Step 1:** Open your scissors and slide the wire about an inch through the place where the blades cross.

**Step 2:** Squeeze the scissors gently. Then, rotate it around the wire a few times or until you can see the metal center. Be careful not to cut the wire!

**Step 3:** Pull off the insulating jacket with your fingers. You've done it!

### C. Battery Holder @ [01-02]


- Insert the black wire (-) at 01 and the red wire (+) at 02.
- Don't insert the batteries yet!

### D. Resistor @ [03-04]

- Insert the ends of the resistor at 03 and 04.
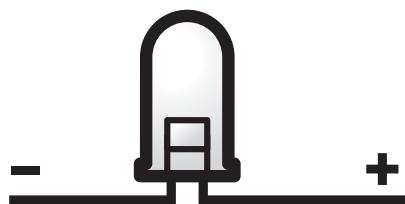
### E. LED bulb @ B [06-07]

- Bend the leads gently until they run flat.
- Mark the longer lead with a black pen.
- Insert the longer lead (+) at 06 and the shorter lead (-) at 07.



## Step 3: Power it UP!

- Insert four batteries into the battery holder and watch the LED light up!

**Remove batteries from holder whenever you're done engineering.**



# THE ELECTRIC PLAYGROUND

Congratulations! You just built your first **basic circuit**. In order to build bigger and more complex ones, you'll need to learn more about the following parts and the rules for forming a circuit. We're off to a great start!

## A basic circuit consists of the following:

- 1 The right **shape** and **materials** for electrons to flow through.
- 2 A **power source** that provides the energy to create electron flow.
- 3 **Other components** that turn electron flow into light, heat, motion, and sound.

## SHAPE


In order for electrons to flow, it needs a path to follow. That's why a basic circuit is formed like a hockey rink. It's a **closed loop** without any gaps or breaks. But when the segments that make up a circuit stop touching, electrons will stop flowing. This is called a **break** in the circuit. Not all breaks are bad though. Have you ever been told by an adult to turn off the lights? If so, you've broken a circuit using a light switch before.

Whether it's a push, pull, or flip, a switch works very much like a Zamboni door because it involves opening and closing a loop for a reason. An open switch usually turns a device off because it creates an **open circuit**. Closing a switch turns a device on. It forms a **closed circuit** so that electrons can flow again.
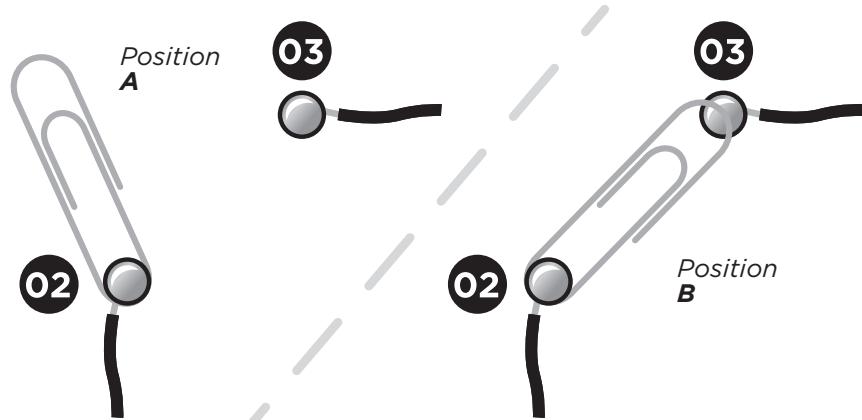
## COACHES CHALLENGE

It's time to add a circuit's version of a Zamboni door to this electric playground. But first, make sure your basic circuit is assembled without any batteries in the battery holder.

**Step 1:** Find a small paper clip.  
**Step 2:** Remove the brass fastener completely at 02 and the wire at [02-03].  
**Step 3:** Insert the brass fastener through one end of the paper clip and push it back into the circuit board at 02. Move the paper clip to position **A**.  
**Step 4:** Insert four batteries into the battery holder.



### Questions:

1. Which of the following circuits did you form with the paper clip at position **A**? Circle the answer below.

2. What will happen to the LED when you move the paper clip to position **B**? Explain.

The LED light should illuminate

OPEN CIRCUIT

or

CLOSED CIRCUIT

Remove batteries from holder whenever you're done engineering.

# THE ELECTRIC PLAYGROUND



## MATERIALS

Circuits must be made of the right materials to give electrons the best chance of flowing through it. That's why **conductors** are often used to form circuits. They're a highway for negative charge! **Insulators**, on the other hand, are often used as a barrier to prevent electrons from flowing to other conductors. Did you know that you can be a conductor if the electricity is strong enough? The rubber layer around an electrical cord is used to keep people, like you, safe from injury.



## COACHES CHALLENGE

There are many objects around the house or classroom that are great conductors and insulators. Are you ready to identify them with your circuit? Complete the following sentence before starting this activity!

A circuit made of *conductors*  
**will** (or) **will not** light the lamp.

A circuit made of *insulators*  
**will** (or) **will not** light the lamp.

**Step 1:** With your circuit built and batteries installed, keep your switch in the OPEN position.

**Step 2:** **Gather** the objects from column A in the chart below.

**Step 3:** **Complete** columns B and C for your first object. Write down what it's made of and predict whether it is a conductor or insulator.

**Step 4:** **Place** the first object onto the brass fasteners at 02 and 03. Make sure they touch both terminals. Did the LED turn on? Update columns D and E.

**Step 5:** **Repeat** step 4 for the rest of the objects.

Object (A)	Material (B)	Prediction (C) (circle one)	LED (D) (circle one)	Results (E) (circle one)
Paper Clip	Metal	Conductor or Insulator	ON or OFF	Conductor or Insulator
Rubber Band	Rubber	Conductor or Insulator	ON or OFF	Conductor or Insulator
Pencil	Rubber, graphite wood	Conductor or Insulator	ON or OFF	Conductor or Insulator
Quarter	Metal	Conductor or Insulator	ON or OFF	Conductor or Insulator
Yarn or String	Cotton	Conductor or Insulator	ON or OFF	Conductor or Insulator
Aluminum Foil	Metal	Conductor or Insulator	ON or OFF	Conductor or Insulator

Results will vary depending on objects but items should behave as noted above



Look around your classroom. List five (5) other objects you think conduct electricity.



# THE STARTING LINE UP

A hockey puck can't reach its potential without the passing, shooting, and stickhandling from Anaheim Ducks players. That's because players have their own abilities to turn the puck into an amazing play leading to a Ducks goal. When Coach Eakins looks at his roster of players each night, he has a very difficult decision to make with his **starting line-up**. He has to choose three **forwards**, two **defensemen**, and one **goaltender** to take the face-off at the start of each game. This decision is an important one because teams that start games well usually wins them.

Are you ready to select your best starting line-up for the next Ducks game? Take a look at what these Anaheim Ducks components can do with the puck!




## #91 Leo Carlsson

Forward / SWE



**Lukas Dostal**

Goalie / CZE

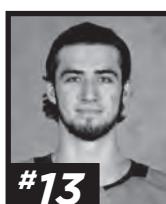

**Nikita Nesterenko**

Forward / USA



**Ryan Strome**

Forward / CAN



**Mason McTavish**

Forward / CHE



**Petr Mrazek**

Goalie / CZE




**Radko Gudas**

Defenseman / CZE



**Drew Helleson**

Defenseman / USA

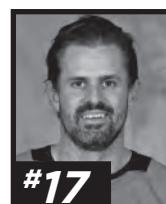

**Alex Killorn**

Forward / CAN



**Chris Kreider**

Forward / USA



**Ryan Poehling**

Forward / USA



**Beckett Sennecke**

Forward / CAN



# THE STARTING LINE UP



## #2 Jackson Lacombe

Defenseman / USA



## LEADER

Controls the game by guiding teammates where to skate to and what to do with the puck.



## DEFENDER

Slows down the puck's movement coming from the opposing team.



## GRINDER

Works hard with and without the puck even with a lot of resistance from opponents.



## DANGLER

Holds the puck on a string using nifty stickhandling moves.



## SPEEDSTER

Plays with the puck at a faster pace than others.

## #19 Troy Terry

Forward / USA

## SNIPER

Shoots the puck with accuracy and power.



#51

Olen Zellweger  
Defenseman / CAN



#61

Cutter Gauthier  
Forward / USA



#64

Mikael Granlund  
Forward / FIN



#65

Jacob Trouba  
Defenseman / USA



#75

Ian Moore  
Defenseman / USA



#77

Frank Vatrano  
Forward / USA



#98

Pavel Mintyukov  
Defenseman / RUS




Daisy  
Team Dog / USA




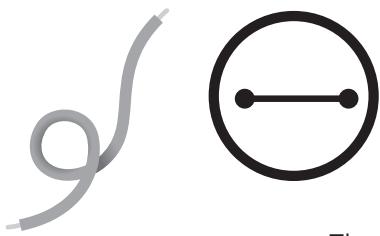
# THE STARTING LINE UP

When it comes to circuits, electrons can't reach their full potential without some important players called **electronic components**. Similar to Ducks players, components come in many different forms, types, and sizes. They also have their own ability to turn electron flow into something useful. Some components can light up a dark room, others are microscopic, and then there are ones that can slow down electron flow with an opposing force called resistance. The best part about components is that you can use many of them in a circuit. You just need to connect them the right way. Once you do, you'll be able to Light the Lamp or accomplish any task with electricity. Let's learn more about the components for your circuit and the important role they play to Light the Lamp. This is your starting line-up!





## Wires- Orange Wire

A wire uses a long piece of conductive material that allows electrons to flow between two points. The orange jacket around the wire is an insulator used to keep electricity from flowing through your hand.
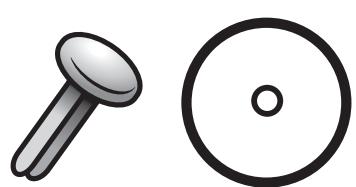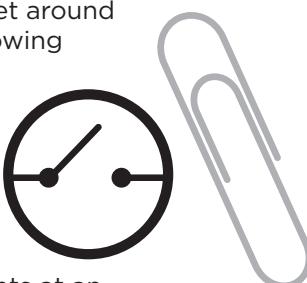
## Switch- Paper Clip

There are many types of switches, but this door like switch uses a metal paper clip to open and close a gap in the circuit.





## Terminal- Brass Fasteners

The brass fastener connects many wires and components at an intersection called a terminal. Most circuit boards use a material called solder in order to accomplish this same task.
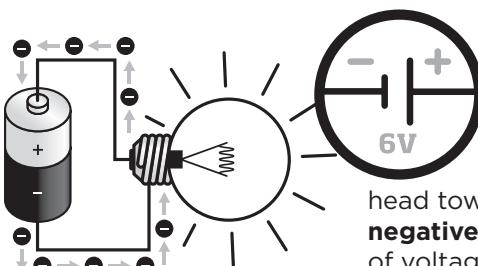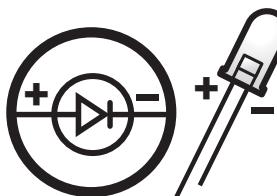
## Light Source- Low Voltage LED

These low-voltage light emitting diodes (LED) turn electron flow into a red light. The long wire is the positive (+) pole and the shorter one is the negative (-) pole. A LED must be connected in the right direction or else it may break.





## Power Source- Four (4) AAA Batteries

Electrons are present in everything but in order for them to start flowing they'll need a power source. A **power source** like a battery uses chemicals to generate the potential energy, or **voltage (v)**, needed to give electrons in a circuit a good push. Once they start flowing, they'll head towards the **positive (+) pole**, or side, of the battery and back out of the **negative (-) pole** so that it can go around the circuit again and again. The amount of voltage you need for a circuit depends on what you want to do.
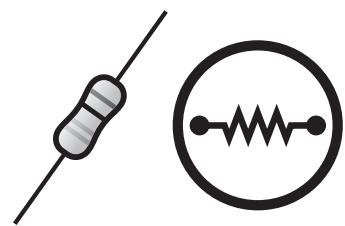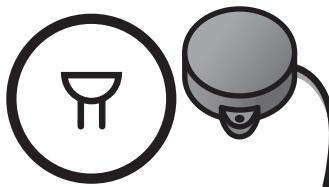
## Sound Source- Buzzer

This buzzer turns electron flow into sound. It uses a magnet and a coil of wire to vibrate a thin sheet of paper. The buzzer will only work if the red wire (+) and black wire (-) are hooked up correctly to the terminals.



## Resistors - $220\Omega$ , $5,000\Omega$ , and $10,000\Omega$

Components can break, or "blow", when the voltage or push from electron flow is too great. When this happens, it's important to add a defensive component called a resistor to the circuit. A resistor's defensive rating, or resistance, is measured in **ohms ( $\Omega$ )**. Therefore, a  $10,000\Omega$  resistor has the ability to slow down electron flow better than a  $220\Omega$  resistor.

-

+

# THE STARTING LINE UP



It's time to watch some great defense against electron flow. Follow the directions below to see the role that resistors play in a circuit.

**Step 1:** Assemble your simple circuit without a resistor.

- **Find** a clear plastic or glass cup.
- **Install** a battery holder with 4 AAA batteries at terminals O1(-) and O2(+).
- **Install** a switch at [O2-O3] and keep it in the OPEN position.
- **Insert** a LED at O6(+) and O7(-).
- **Insert** wires at all other segments [O3-O4], [O4-O5], [O5-O6], [O7-O8], [O8-O9], and [O1-O9] to complete the circuit.
- **Place** the cup over the LED. This is for safety!

**Step 2:** Turn on your circuit.

- **Swing** the paper clip to the CLOSE position so that it touches the brass fastener at O3. Keep your circuit on for at least 30 seconds.
- **Record** your findings in the chart below. Measure the brightness of the LED (0-no light; 10-very bright). Then, write down what you saw in the notes column.

**Step 3:** Let's ADD a defensive force!

- **Turn off** your circuit to the OPEN position (remove the cup over the LED if it's still there).
- **Replace** the wire at [O3-O4] with a  $220\Omega$  resistor.
- **Turn on** your circuit and record your findings in the chart below.

**Step 4:** Let's INCREASE the defensive force!

- **Repeat** step 3 with a  $5,000\Omega$  resistor (green, brown, black, brown, brown) and then a  $10,000\Omega$  resistor (brown, black, black, red, brown).

Resistor	LED Brightness	Notes
None	0 1 2 3 4 5 6 7 8 9 10	
$220\Omega$	0 1 2 3 4 5 6 7 8 9 10	
$5,000\Omega$	0 1 2 3 4 5 6 7 8 9 10	Answers will vary
$10,000\Omega$	0 1 2 3 4 5 6 7 8 9 10	

## QUESTIONS

1. Why do you think the LED stopped working when there were no resistors connected to the circuit? *Explain.*

**Components can break, or "blow", when the voltage or push from electron flow is too great**

2. According to your findings, how did replacing the resistors affect the LED? What do you think would happen to the LED (and circuit) if you continued to add more resistance? *Explain.*

**Lights should dim. Eventually, enough resistance would restrict electron flow to the LED and it would not illuminate.**




**Don't forget to remove the batteries when you're done!**


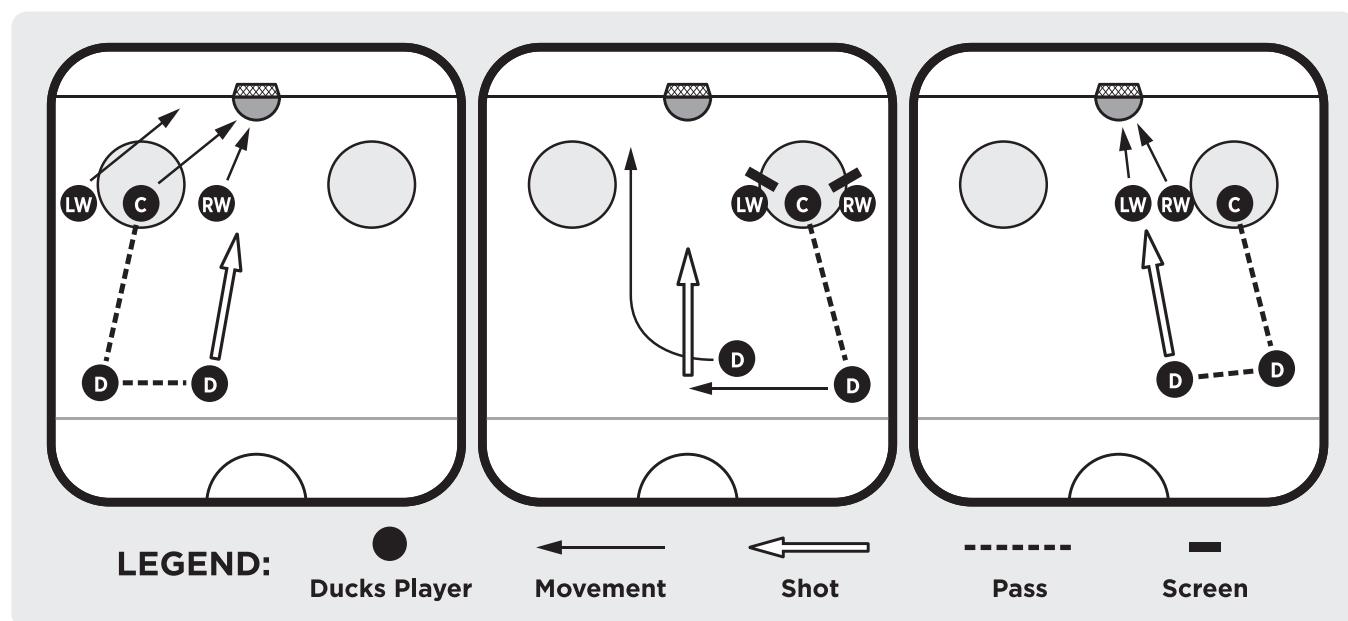
# DRAWING IT UP


In hockey, a team is given only one timeout. It's a 30-second stop in the game coaches use to speak to players or give them a quick rest. That's why this important timeout is often saved for the final minutes when a game tying goal or a key defensive stop is needed. During a timeout, players huddle around their coach as he draws shapes, symbols, and lines on a white board. This is called **drawing up a play**. They are instructions showing players where to stand, who to pass to, and where to skate to once the puck is dropped. Check out some of the hockey plays Coach Eakins has drawn up in the past that have led to some exciting Light the Lamp moments.



Drawing a **circuit diagram** is similar to drawing up a play in hockey. It uses a variety of shapes, symbols, and lines to represent a circuit that you want to build. These diagrams help engineers know which components to use, where to place them, and how to connect them to form the circuit. To learn how to draw one of these helpful pictures, take a look at the following steps that were taken to create a diagram for the circuit on page 10.




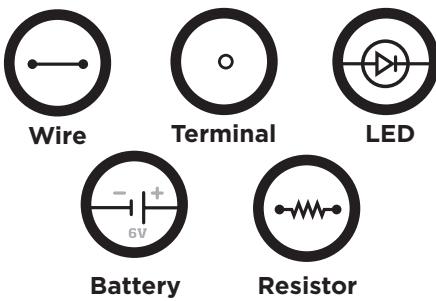symbol so that you can draw them. They can be found on page 16 of this workbook.



**Step 1:** Identify the components you want to build a circuit with. You'll need to know their

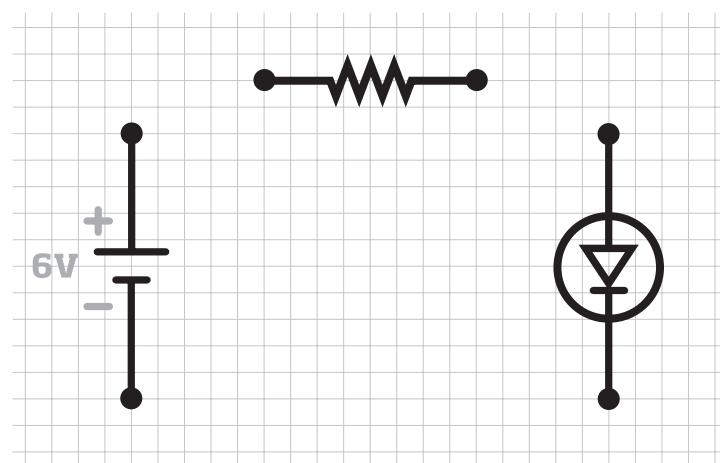
**Step 2:** Place your components by drawing them into position.


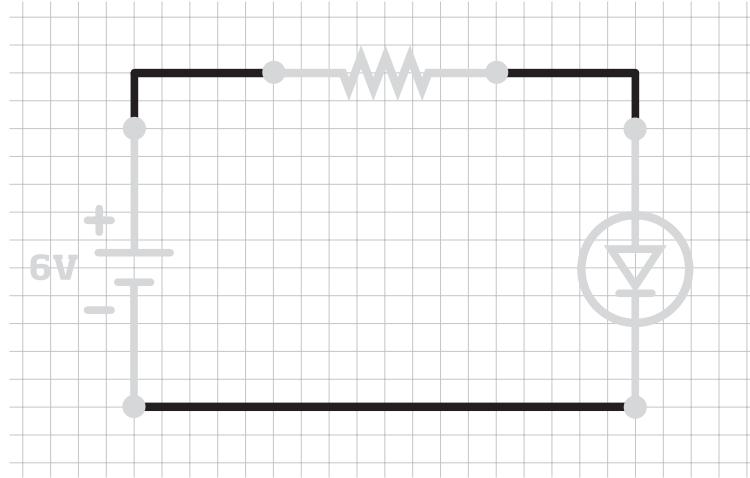
# DRAWING IT UP



**Step 3:** Connect the components with lines to complete the circuit. You can draw them in any way you wish to. However, engineers draw straight lines for a cleaner look so that others seeing this picture can know exactly how to build the circuit.



In the space below, use the three steps to draw a circuit diagram for the circuit on page 12.

**\*\*Illustrations will vary\*\***

Hey! Come over  
here! We're talking  
about circuits.





# DRAWING IT UP

Another reason engineers draw circuit diagrams is because circuits can get quite complicated once you start adding more “players”. This tool comes in handy whether you want to add a few components or even thousands of them. And it’s even more important to use when they’re connected in series or parallel.


## SERIES CIRCUIT

A **series circuit** connects every component in a single path. Electrons flow through one component, then the next, and continues to do this until it makes its way around to the battery. This type of connection is very simple to build but it has some drawbacks. For instance, connecting two LED bulbs in series will be half as bright than a circuit with only one LED bulb. The voltage drops off, or decreases, each time electrons flow through a component. Also, if a component breaks, the entire series circuit will turn off.



Build the following circuits to see how components, like red LED bulbs, work when they are connected in series. Use terminals 01 to 09 for this activity.

### Series Circuit Examples

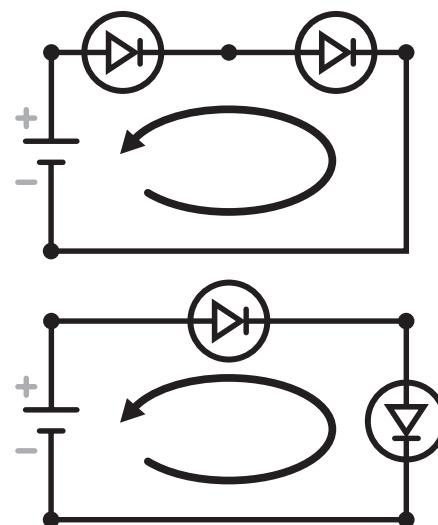

### One LED Bulb Simple Circuit

- Step 1: **Assemble** the circuit from page 12 with the switch in the OPEN position.
- Step 2: **Turn on** the circuit.
- Step 3: **Measure** the brightness of the bulb and record it in the chart (0-no light; 10-very bright).

### Two LED Bulb Series Circuit

- Step 1: **Turn off** the circuit to the OPEN position.
- Step 2: **Remove** the components from **A** [05-06], **B** [06-07], and **C** [07-08].
- Step 3: **Attach** the following components:
  - Wire segment at **B** [06-07].
  - LED bulbs at **A** [05-06] and **C** [07-08]. Make sure the longer leads (+) for each LED are connected to 05 and 07.
- Step 4: **Turn on** the circuit.
- Step 5: **Measure** the brightness of the bulbs at **A** and **C** and record them in the chart.

### Questions:

1. Compare the LED bulbs between the simple and series circuits. What caused them to light up differently?

In a series circuit, two LED bulbs will be half as bright. The voltage drops off or decreases each time electrons flow through a component

2. How would the LED bulbs in the series circuit change if a third LED was added? Explain.

(HINT: Replace the wire at **B** [06-07] with an LED.)

The lights would dim even further as electrons flow would decrease through each component

3. What would happen to the series circuit if one of the LED bulbs was removed?

(HINT: Remove a LED bulb while the circuit is on.)

The circuit would be broken (open) and no component would illuminate.

# DRAWING IT UP



## PARALLEL CIRCUIT

In a **parallel circuit**, electrons follow multiple paths. When a circuit splits, some electrons will follow one path while the rest will flow into the other ones. Although this happens, electrons will always meet back up and return to the battery together. Parallel circuits take more time to set up but they have an important feature that's advantageous to use. They can continue to work even if a component in one path breaks. That's why long strands of holiday lights are formed this way. It can continue to decorate your home even when a bulb goes out.



Build the following circuit to see how components, like red LED bulbs, work when they are connected in parallel. Follow the directions carefully because this circuit is unlike anything you've seen before!

### Two LED Bulb Parallel Circuit

**Step 1: Turn off** the circuit to the OPEN position.

**Step 2: Remove** the components from **A** [05-06], **B** [06-07], and **C** [07-08].

**Step 3: Attach** the following components:

- Wire segments at [05-10], [10-11], [10-13], [12-15], [14-15], and [08-15].
- 220Ω resistor at [03-04].
- LED bulbs at **D** [11-12] and **E** [13-14]. Make sure their longer leads (+) are connected to 11 and 13.

**Step 4: Turn on** the circuit.

**Step 5: Measure** the brightness of the bulbs at **D** and **E** and record them in the chart.

#### Questions:

1. Compare the brightness of the LED bulbs formed in simple, series, and parallel circuits. What did you see?

**Students should refer to the chart below to record their observations and brightness**

2. What would happen to the circuit if one of the LED bulbs was removed? *Explain.*



**(HINT:** Go ahead and pull out one LED bulb!)

**The other light continues to remain illuminated. Parallel circuits can continue to work even if one path breaks.**

## CHART

Formation	# of LED	Brightness
Simple Circuit	1	<b>LED @ B:</b> 0 1 2 3 4 5 6 7 8 9 10
Series Circuit	2	<b>LED @ A:</b> 0 1 2 3 4 5 6 7 8 9 10 <b>LED @ C:</b> 0 1 2 3 4 5 6 7 8 9 10
Parallel Circuit	2	<b>LED @ D:</b> 0 1 2 3 4 5 6 7 8 9 10 <b>LED @ E:</b> 0 1 2 3 4 5 6 7 8 9 10

### Parallel Circuit Examples

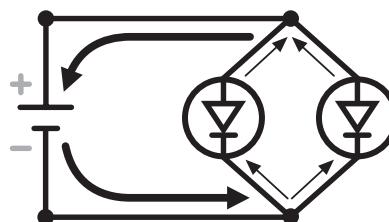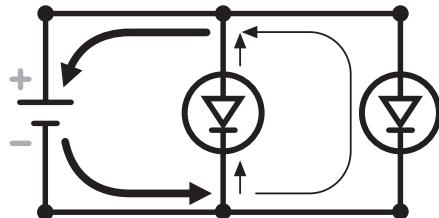

**Don't forget to remove the batteries when you're done!**



# THE CHALLENGE

Congratulations. You did it! But even as a new engineer who has just harnessed the powers of electricity, your journey is not over. In fact, it gets better. The best part of being an engineer isn't learning about math formulas or electricity concepts. Instead, it's about using all of this information to think BIG! Every day, engineers answer the call to improve on past inventions, build the next cool gadget, or make things that help others in need. Are you ready to take on this challenge when it comes to hockey? Here are some easy steps called **The Engineering Design Process** that will help you Light the Lamp creatively. We can't wait to see you innovate!

*Use your journal to take notes or write down ideas that will help improve your Light the Lamp circuit.*

## STEP 1: ASK A QUESTION

Thinking big always starts with a big question that deals with the problem to solve or an object to improve upon. **What can you do to make the Light the Lamp circuit bigger and better?**

## STEP 2: BRAINSTORM

Work alone or with a large group to create a list of ideas and write them all down in a journal or on a whiteboard. Remember, all ideas are good ideas! **What ideas do you have in your head?**

## STEP 3: DESIGN

Take your best ideas and decide on the best solution. Then, draw pictures and circuit diagrams to create the plans for how it will be built. **What are you going to design and how will it be made?**

## STEP 4: BUILD, TEST, & REDESIGN

Assemble your circuit and watch it come to life. If it doesn't work, don't worry. Even the best electrical engineers have to go back to the drawing board. **How will you build, test, and improve your design?**

## STEP 5: SHARE!

Don't keep your design a secret! Imagine a world where no one shared their ideas. There wouldn't be life-saving medical equipment or spacecraft to explore the Universe. Share your work in a report, through a presentation, or using technology like videos or apps. **How will you share your work with others?**

# THE CHALLENGE



# Waste to Watts

*Presented by*



## FROM THE LANDFILL TO THE GOAL LAMP

When the Anaheim Ducks score a goal, the goal lamp lights up thanks to electricity. Did you know that the landfills operated by OC Waste & Recycling also help to make electricity using buried organic waste? At the landfill, leftover food and yard waste break down and make a gas called methane. Instead of releasing this harmful greenhouse gas into the atmosphere, we collect it and use it to power a Renewable Gas Plant (the RNG Plant) that turns it into renewable energy. Just like the goal lamp lights up the rink, this renewable gas can help light up homes, schools, and even the Honda Center!

But the real win happens when we all work as a team. At home, make smarter choices by putting food scraps and yard waste in the green organics bin. At the landfill, facilities like the RNG Plant capture methane and turn it into clean energy—turning today's waste into tomorrow's power for a greener, healthier Orange County.

### HOW IT WORKS...



#### 1. Trash Makes Gas

When food scraps and yard waste get buried in the landfill, they break down and make a gas called methane, which is a greenhouse gas and can be harmful to the environment.




#### 2. Pipes Collect the Gas

At OC landfills, a network of underground pipes collects the methane and sends it to the RNG Plant. There, the gas is cleaned so it's safe to use.


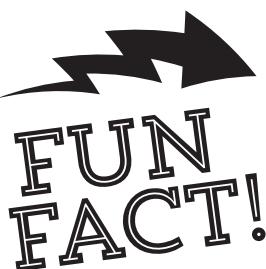
#### 3. Gas Makes Electricity

The clean gas is sent into big engines at the RNG Plant. When the gas is burned, the engines run—just like an internal combustion car engine—and that motion creates electricity to power homes and schools in Orange County.



Every year, the Frank R. Bowerman Landfill's RNG plant produces **23 megawatts of electricity!**

### Want to make a difference at home and school?

Visit [OCLandfills.com/ProjectZeroWaste](http://OCLandfills.com/ProjectZeroWaste) for activities and to register for the County of Orange's free Project Zero Waste program.





PRESENTED BY  | UCI Health

**OFFICIAL SOUVENIR OF THE  
FIRST FLIGHT FIELD TRIP**

BECOME A MEMBER OF THE WILD WINGS KIDS CLUB AND TAKE HOME A LIMITED EDITION WILD WING T-SHIRT, OFFICIAL MEMBERSHIP CARD, SOUVENIR HAT, COUPON FOR ONE FREE CHICK-FIL-A KIDS MEAL, AND ONE FREE PUBLIC ICE SKATING PASS!


**ORDER NOW FOR ONLY \$25!**



SCAN HERE TO ORDER

SOUVENIR PACKS WILL BE SHIPPED DIRECTLY TO YOUR SCHOOL.

# HOCKEY HOMEWORK!

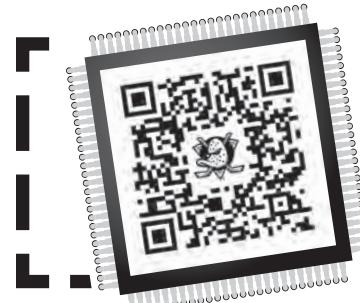

**The Anaheim Ducks want to invite you to Honda Center to watch a game live!**

Take this workbook home so your family can scan the QR code to receive up to **18% OFF** per ticket on select regular season home games.

Whether you're in the arena, in your classroom, or at home, take some time to put what you've learned about hockey to the test!

## WATCH AND LEARN!

Watch the Ducks practice, turn on a game live, or search some clips to help you answer the tickets below.

How many players are on the ice for one team during regular play?

**6, 5 skaters and 1 goalie**

There are three main positions, what are they?

**Foward, Defense, Goalie**

What is it called when the ref drops the puck to start play? **HINT:** look at how the teams are facing each other.

**Faceoff**

What happens after a player takes a penalty?

**They sit in the penalty box**

Watch the play clock, how many passes and you count the Ducks make in one minute?

**Answers will vary**

How do you earn points and win the hockey game?

**Put the puck in the net to score a goal. Score more goals than the other team.**




## WANT TO WATCH THE GAME LIVE?

Scan the QR code to see when the Ducks play.

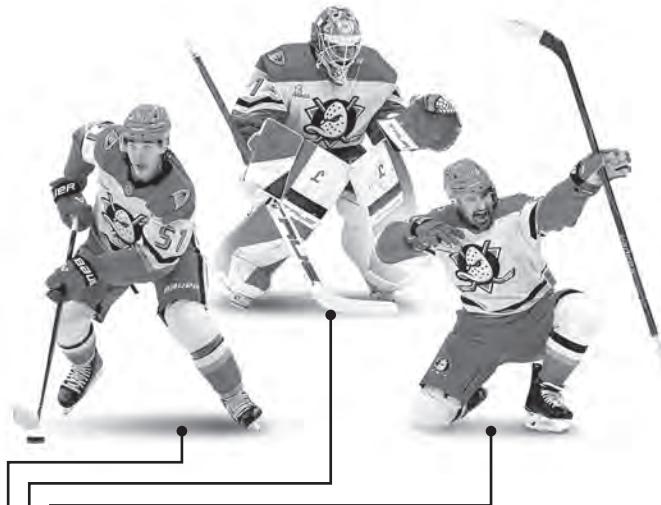**Watch free on the Victory+ app!**

Refer to the roster section on pages 14 and 15. Can you identify these players and their positions?



Player Name: **Chris Kreider**

Player Position: **Foward**

Player Name: **Lukas Dostal**

Player Position: **Goalie**

Player Name: **Olen Zellweger**

Player Position: **Defense**



# CHECK THE MATH!

These questions are written for 3rd through 6th graders. Some might be easy for you, and some might be hard, but we can do hard things! Ask your teammates (*classmates*) and coaches (*teachers*) for help. After each question identify if you thought it was **easy** or **hard**!

1. The Ducks take 12 shots in the first period and 17 shots in the second period. How many total shots do they have after two periods?

29

---

**EASY** or **HARD**

2. Troy Terry wears number 19 on the back of his jersey. Leo Carlsson wears number 91 and Kris Kreider wears number 20. What's the total sum of their jerseys numbers?

130

---

What's the difference between the highest and lowest jersey number?

72

---

**EASY** or **HARD**

3. There are 21,879 fans in Honda Center, if 10,000 of them leave early, how many fans remain in Honda Center?

11,873

---

**EASY** or **HARD**

4. The referee uses 12 new hockey pucks a period. There are 3 periods in a hockey game. How many hockey pucks does the referee use in the whole game?

36

---

**EASY** or **HARD**

5. A hockey stick is 60 *inches* long. How many *feet* long is it? **HINT:** 12 *inches* = 1 *foot*

5ft

---

**EASY** or **HARD**

6. There are 18 players on the bench. If 6 go onto the ice at once, what fraction of the players are now skating?

6/18, 1/3

---

What fraction remain on the bench? Reduce to lowest common denominator

12/18, 2/3

---

**EASY** or **HARD**



# I SPY - FROM MY SEAT!



**Whether you're in Honda Center or your classroom, take a second to look around. What do you see? Can you find some things listed below?**

How many Ducks logos  **DUCKS** can you find in the arena or your classroom?

**Answers will vary**

What is the temperature like? Are you cold? Are you warm?

**Answers will vary**

Can you see any national flags? If so, what country are they from?

**USA and Canada**

How many people are around you? Can you count them?

**Answers will vary**

Can you come up with your own **H O C K E Y** team names?

H awks (example)

O  

C  

**Answers will vary**

K  

E  

Y  

*Man, who knew there was so much to learn about hockey?*



**Sad you've completed the First Flight workbook?  
Don't be! Continue the fun learning at Discovery Cube!** Scan here for more information!

Teachers, book your class a field trip **starting at just \$11 per student!**



DiscoveryCube





# WORD INDEX

<b>Amperes</b>	The measurement of rate or speed of electron flow.
<b>Atom</b>	Small building blocks that make up everything we see.
<b>Circuit</b>	A complete, closed loop that allows electrical current to flow through it.
<b>Closed Circuit</b>	An electrical circuit that is complete and allows electrons to pass through.
<b>Conductors</b>	A material that allows electricity to flow through it with low resistance.
<b>Current Electricity</b>	A continuous or non-stop flow of electrons through an object.
<b>Defenseman</b>	A player on the team whose job is to prevent the opposing team from scoring goals.
<b>Electricity</b>	<ol style="list-style-type: none"><li>1. A form of energy resulting from the existence of charges particles such as electrons or protons.</li><li>2. A state or feeling of thrilling excitement.</li></ol>
<b>Electron</b>	A subatomic particle with a negative electric charge found in the nucleus of every atom.
<b>Engineer</b>	A person who designs, builds, or maintains machines, structures, or systems.
<b>Even-Strength</b>	When both hockey teams are playing with the same amount of players.
<b>Faceoff</b>	When two teams face each other and the referee drops the puck to start play.
<b>Forward</b>	A player on the team whose job is to score goals.
<b>Goaltender</b>	The player who stays in the net and only job is to stop the puck from going in the net.
<b>Ice Rink</b>	The surface or arena where a hockey game is played.
<b>Innovate</b>	Make changes in something established, especially by introducing new methods and ideas.
<b>Insulators</b>	A barrier that prevents electrons from flowing to another conductor.
<b>Neutron</b>	A subatomic particle without an electric charge.
<b>Open Circuit</b>	An electrical circuit that is not complete where electrons do not pass through.
<b>Parallel Circuit</b>	An electrical circuit where multiple components are connected across the same two points.
<b>Penalty Kill</b>	When one team is playing with one less player than the other team.
<b>Power Play</b>	When one team is playing with one more player than the other team.
<b>Proton</b>	A subatomic particle with a positive electric charge found in the nucleus of every atom.
<b>Reverse Engineering</b>	The process of solving a problem backwards.
<b>Static Electricity</b>	A buildup of electrons on the surface of an object.
<b>Terminals</b>	A place where wires and components connect to allow electricity to pass through.

THE ANAHEIM DUCKS  
WOULD LIKE TO THANK THE  
FOLLOWING FOR THEIR SUPPORT  
OF THE FIRST FLIGHT FIELD TRIP



**FUTURE  
GOALS**<sup>TM</sup>

POWERED BY EVERFI



**DiscoveryCube**  
OC & LA



LONG LIVE CHILDHOOD



**ANAHEIM DUCKS  
FOUNDATION**



**OC** COUNTY OF ORANGE  
Waste & Recycling  
*Our Community. Our Commitment.*

